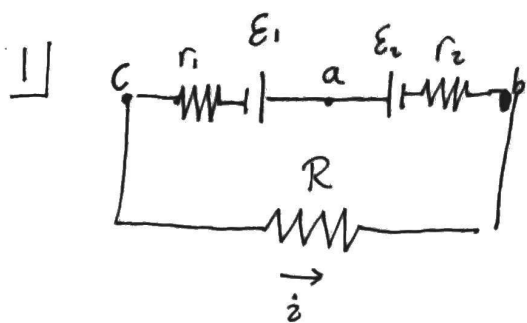


12 DC Circuits - Resistors and Batteries



(a) i is the same everywhere in the circuit, because there are no branches.

(All junctions are like $i_{in} \rightarrow i_{out} \Rightarrow$ Apply 1st Law)

Loop rule:



Batteries: $-\mathcal{E}_1, +\mathcal{E}_2$

Resistors: $-i r_2, -i R, -i r_1$

$$-\mathcal{E}_1 + \mathcal{E}_2 - i(r_2 + R + r_1) = 0$$

Solve for I :


$$i = \frac{\mathcal{E}_2 - \mathcal{E}_1}{r_1 + r_2 + R}$$

Alternatively:



$$\cong \text{---} \mathcal{E}_2 - \mathcal{E}_1 \text{---}$$

(Batteries in series)

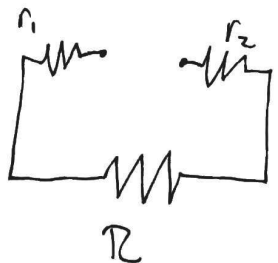


$$\cong \text{---} r_1 + r_2 + R \text{---}$$

(Resistors in series)

$$\Rightarrow i = \frac{\mathcal{E}_{eff}}{R_{eff}} = \frac{\mathcal{E}_2 - \mathcal{E}_1}{r_1 + r_2 + R}$$

(b) Between points a and b:

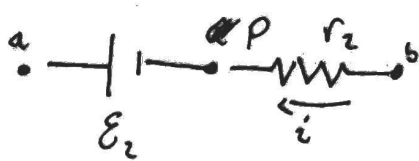


$$V_a - V_P = \mathcal{E}_2$$

$$V_b - V_P = i r_2$$

$$\Rightarrow V_a - V_b = \mathcal{E}_2 - i r_2$$

(c) Between points a and c:

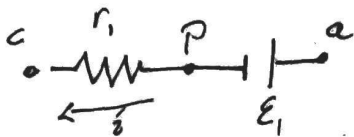


$$V_a - V_P = \mathcal{E}_1$$


$$V_P - V_c = i r_1$$

$$\Rightarrow V_a - V_c = \mathcal{E}_1 + i r_1$$

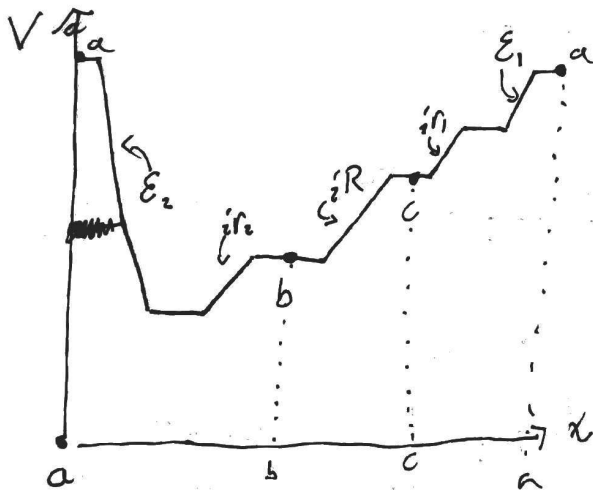(d) (Assuming $\mathcal{E}_2 - \mathcal{E}_1 > 0$, so $i > 0$ - that is, picked correct direction for i)



(b) Between points a and b:

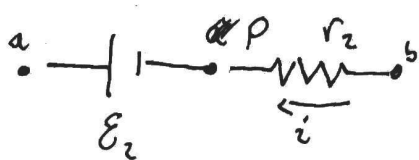


$$V_a - V_p = \mathcal{E}_2$$

$$V_b - V_p = i r_2$$

$$\Rightarrow V_a - V_b = \mathcal{E}_2 - i r_2$$

(c) Between points a and c:

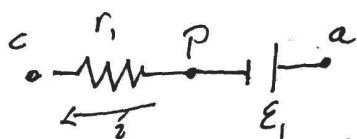


$$V_a - V_p = \mathcal{E}_1$$


$$V_p - V_c = i r_1$$

$$\Rightarrow V_a - V_c = \mathcal{E}_1 + i r_1$$

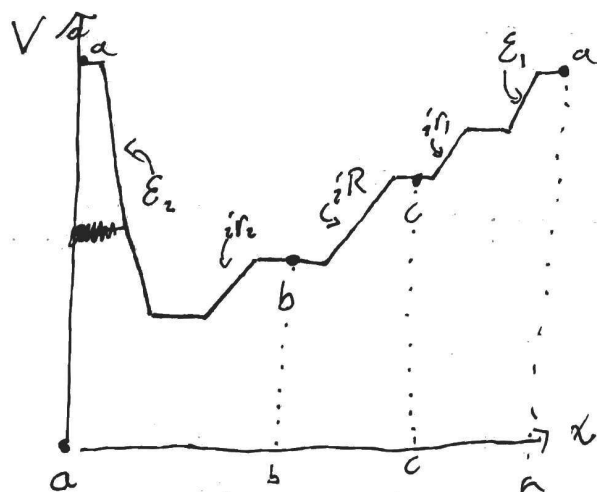(d) (Assuming $\mathcal{E}_2 - \mathcal{E}_1 > 0$, so $i > 0$ - that is, picked correct direction for i)




2]

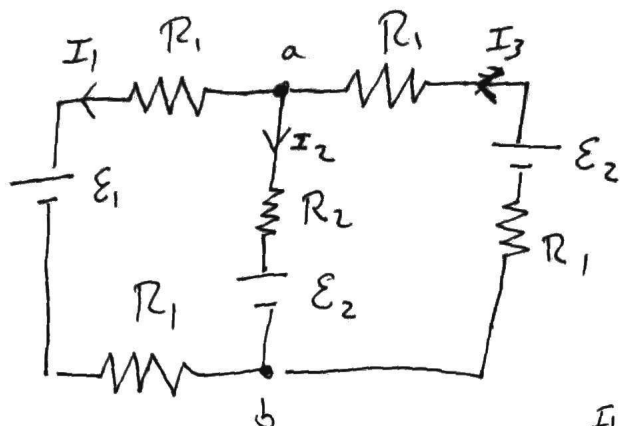

(a) In this problem, we'll use Kirchhoff's rules.

Junction rule: $I_3 = I_1 + I_2$

Loop rule (2 of them):

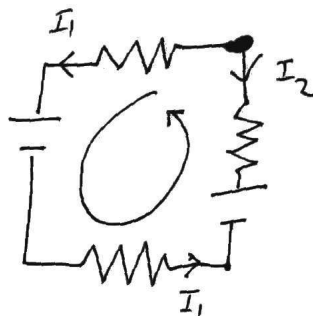


$$\begin{aligned} \mathcal{E}_1 &= 2 \\ \mathcal{E}_2 &= 6 \\ R_1 &= 2 \\ R_2 &= 4 \end{aligned}$$

$$\begin{aligned} 0 &= -I_1 R_1 - \mathcal{E}_1 - I_1 R_1 + \mathcal{E}_2 + I_2 R_2 \\ &= (\mathcal{E}_2 - \mathcal{E}_1) - 2 I_1 R_1 + I_2 R_2 \\ &= 4 - 4 I_1 + 4 I_2 \end{aligned}$$

$$\cancel{1/I_1} \quad I_1 = I_2 + 1 \quad \Rightarrow \quad I_3 = 2I_2 + 1$$

Second loop:

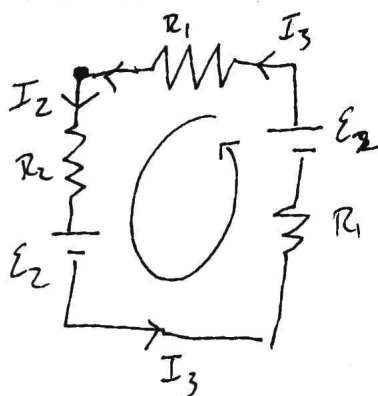

$$\begin{aligned} 0 &= -I_2 R_2 - \mathcal{E}_2 - I_3 R_1 + \mathcal{E}_2 - I_3 R_1 \\ &= -I_2 R_2 - 2 I_3 R_1 \end{aligned}$$

$$0 = 4 I_2 + 4 I_3$$

$$\Rightarrow I_2 = -I_3 = -2 I_2 - 1$$


$$\Rightarrow \boxed{I_2 = -1/3} \text{ A}$$

$$\Rightarrow \boxed{I_1 = 1 + I_2 = +2/3}$$

$$\Rightarrow \boxed{I_3 = I_1 + I_2 = 1/3}$$


(All in amps)
if $\mathcal{E} \sim \text{volts}$
 $R \sim \text{ohms}$

(b)

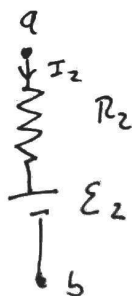

$$V_a - V_b = I_2 R_2 + \mathcal{E}_2 = -\frac{1}{3} \cdot 4 + 6 = \frac{14}{3}$$

3

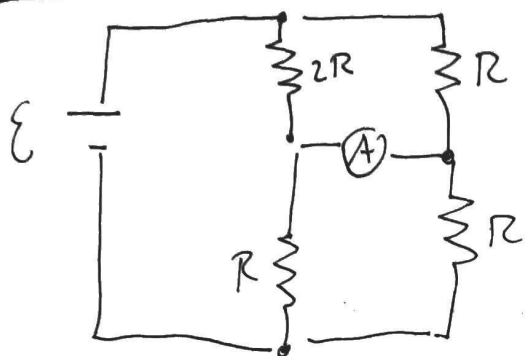


What is the current through \textcircled{A} ?
 \uparrow 0 resistance

This problem can be solved by applying Kirchhoff's laws, though it ends up being a bit tedious.


Instead, we use a trick.

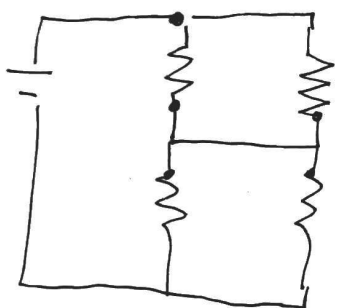Since \textcircled{A} has zero resistance, replace it w/ ideal wire:




Because connected by ideal wires, everything in this area at same potential.

Can rearrange like:

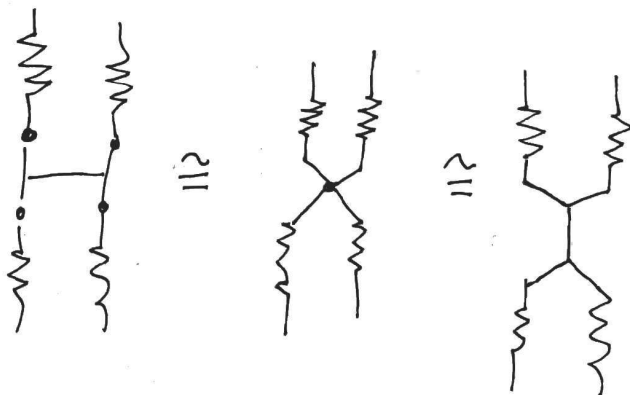


3, continued

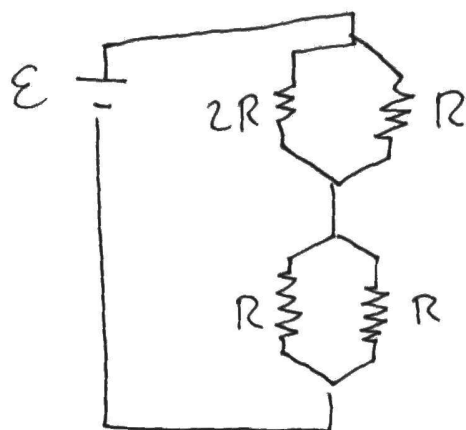So really the circuit is equivalent to a series/parallel:



Combine
Parallel
 \approx

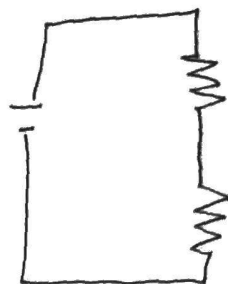

$$(R^{-1} + \frac{1}{2} R^{-1})^{-1} = \frac{2}{3} R$$

$$(R^{-1} + R^{-1})^{-1} = \frac{1}{2} R$$


Series
 \approx



$$R_{\text{eff}} = \frac{1}{2} R + \frac{2}{3} R = \frac{7}{6} R$$

\Rightarrow Current coming out of battery is $I_0 = \frac{\epsilon}{R_{\text{eff}}} = \frac{6}{7} \frac{\epsilon}{R}$


Now we work backwards:

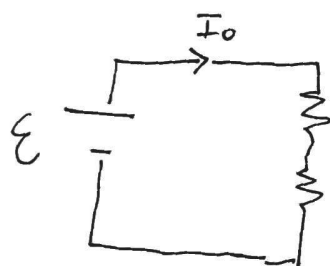

$$\Rightarrow V_1 = \frac{2}{3} I_0 R = \frac{4}{7} \epsilon$$

$$\Rightarrow V_2 = \frac{1}{2} I_0 R = \frac{3}{7} \epsilon$$

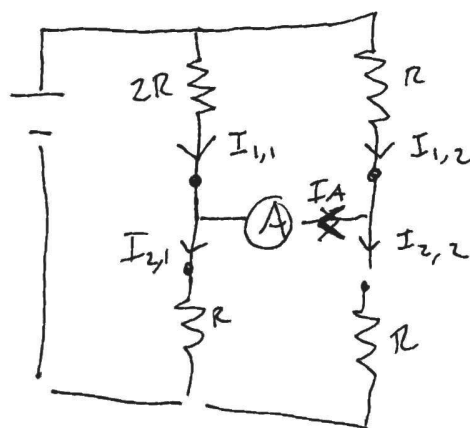With these
voltage diff,
find currents through
each resistor.



$$I_{1,1} = V_1 / 2R = \frac{2}{7} \frac{\epsilon}{R}$$

$$I_{1,2} = V_1 / R = \frac{4}{7} \frac{\epsilon}{R}$$

$$I_{2,1} = I_{2,2} = V_2 / R = \frac{3}{7} \frac{\epsilon}{R}$$

* Law:
Junction
rule

$$I_A = I_{2,1} - I_{1,1} = \frac{3}{7} \frac{\epsilon}{R} - \frac{2}{7} \frac{\epsilon}{R}$$

$$= \boxed{\frac{1}{7} \frac{\epsilon}{R}}$$